



Dr. Bonnie H. Ferri
Professor and Associate Chair
School of Electrical and
Computer Engineering

Introduction to Electronics

An introduction to electronic components and a study of circuits containing such devices.

TECH



Dr. Bonnie H. Ferri
Professor and Associate Chair
School of Electrical and
Computer Engineering

Review of Circuit Elements

Review linear circuit components and properties

TECH


Lesson Objectives

⦿ Review

- Resistors, capacitors, inductors
 - i-v characteristics of these elements
- Sources, nodes


Passive Elements

Resistor

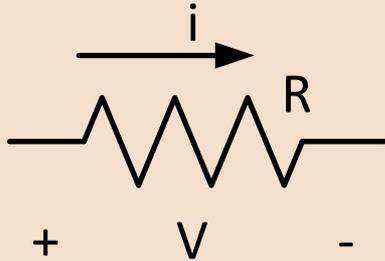


$$V = iR$$

Capacitor

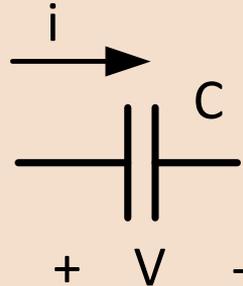




$$i = C \frac{dV}{dt}$$

Inductor

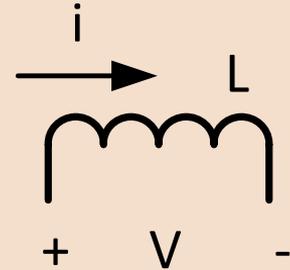


$$V = L \frac{di}{dt}$$



Series and Parallel Connections

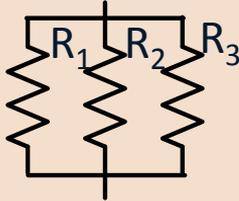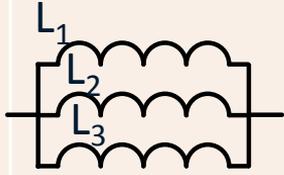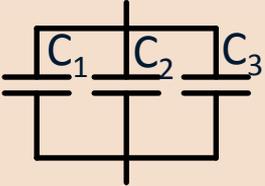	Series	Parallel
Resistors	 $R = R_1 + R_2$	 $R = \frac{1}{\frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3}}$
Inductors	 $L = L_1 + L_2$	 $L = \frac{1}{\frac{1}{L_1} + \frac{1}{L_2} + \frac{1}{L_3}}$
Capacitors	 $C = \frac{1}{\frac{1}{C_1} + \frac{1}{C_2} + \frac{1}{C_3}}$	 $C = C_1 + C_2 + C_3$

Connections and Sources

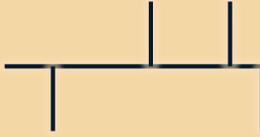Ground	 <p>Reference for 0 volts</p>	
Node	 <p>Voltage level the same everywhere on the node</p>	
Voltage Source	<p>Independent</p> 	<p>Dependent</p> 
Current Source	<p>Independent</p> 	<p>Dependent</p> 

Circuit Connections

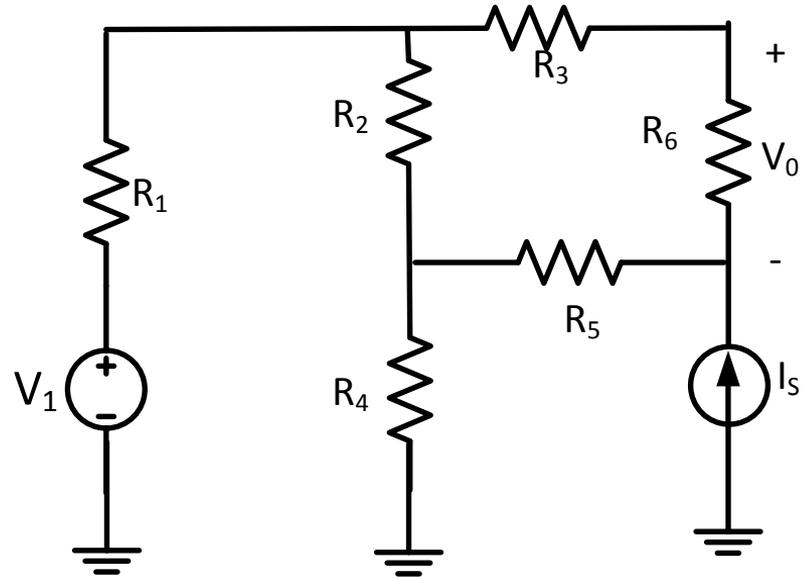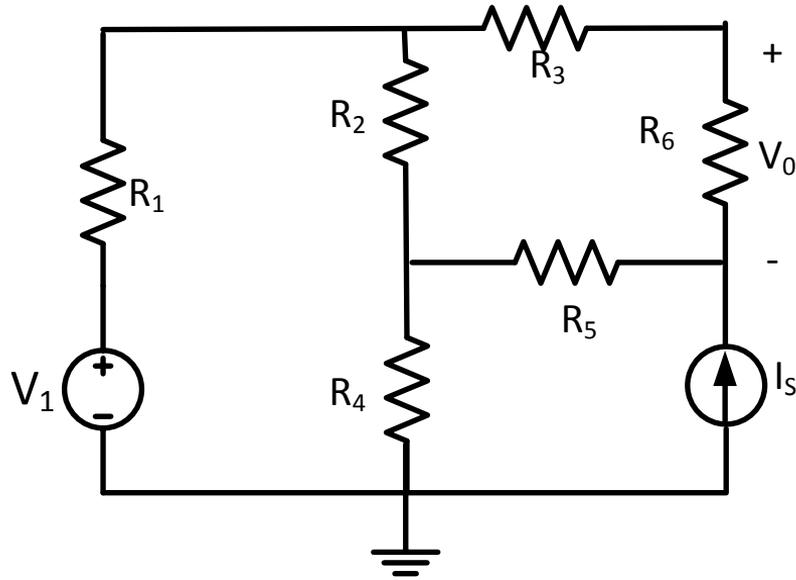

Next Lesson

- Review of Kirchhoff's Laws