



Dr. Bonnie H. Ferri
Professor and Associate Chair
School of Electrical and
Computer Engineering

Introduction to Electronics

An introduction to electronic components and a study of circuits containing such devices.

TECH



Dr. Bonnie H. Ferri
Professor and Associate Chair
School of Electrical and
Computer Engineering

Review of Frequency Response Plots (Bode)

Review of linear plots and Bode plots to show the frequency characteristics of signals and circuits

TECH

Previous Lesson

- ⦿ Review of Transfer Functions



Lesson Objectives

- Define the frequency response for a transfer function $H(\omega)$

Magnitude Plot: $|H(\omega)|$ vs ω
Angle Plot: $\angle H(\omega)$ vs ω

- Show linear plots and Bode plots

Frequency Response

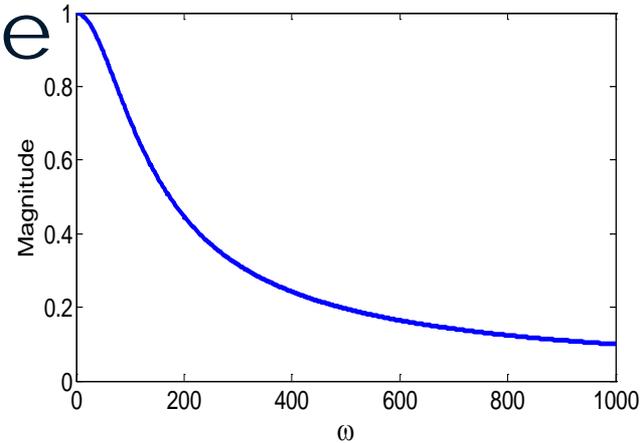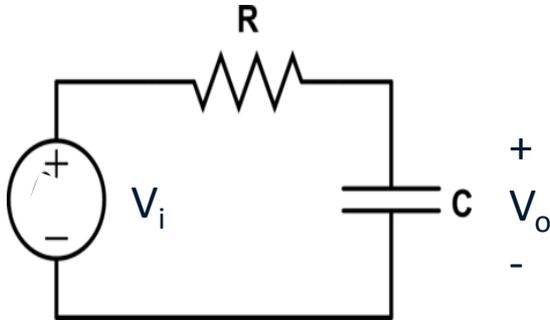


Transfer Function




$$H(\omega) = \frac{1}{1 + RC\omega j}$$

$$|H(\omega)| = \frac{1}{\sqrt{1 + (RC\omega)^2}}$$
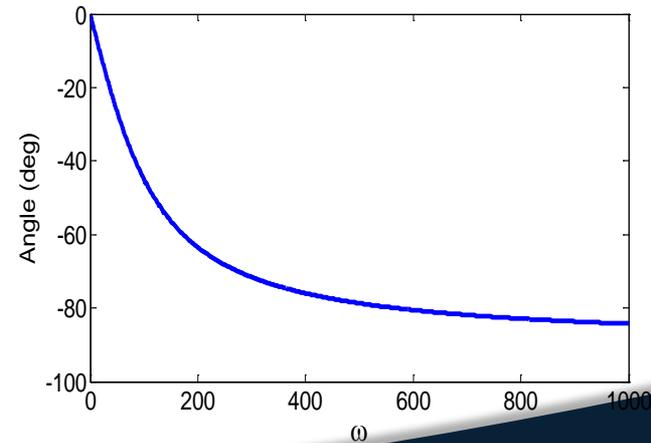
$$\angle H(\omega) = -\text{atan}(RC\omega)$$





Circuit Response

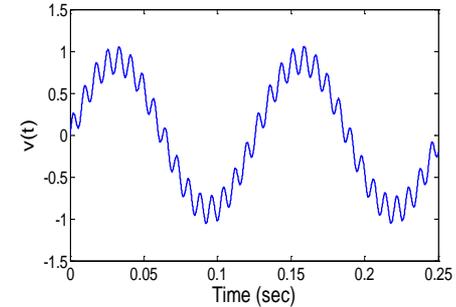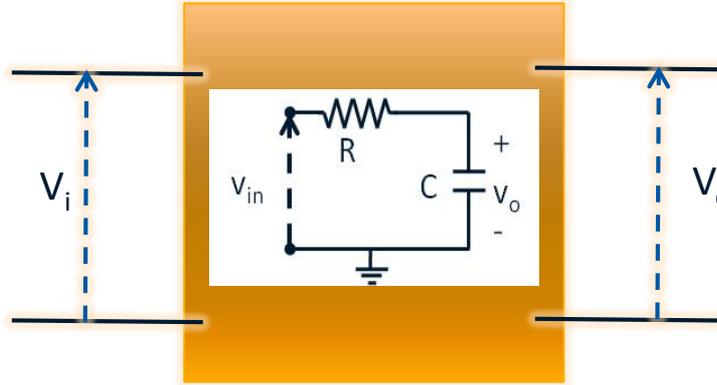
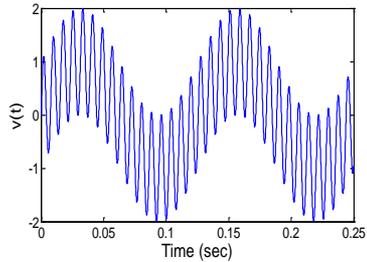


$$V_i = \cos(50t) + \cos(800t)$$



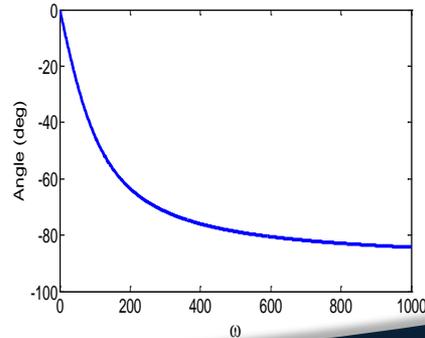
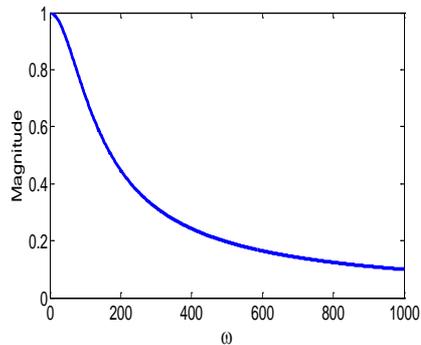
$$V_o = 0.95\cos(50t-20^\circ) + 0.13\cos(800t-85^\circ)$$




Bode Plots

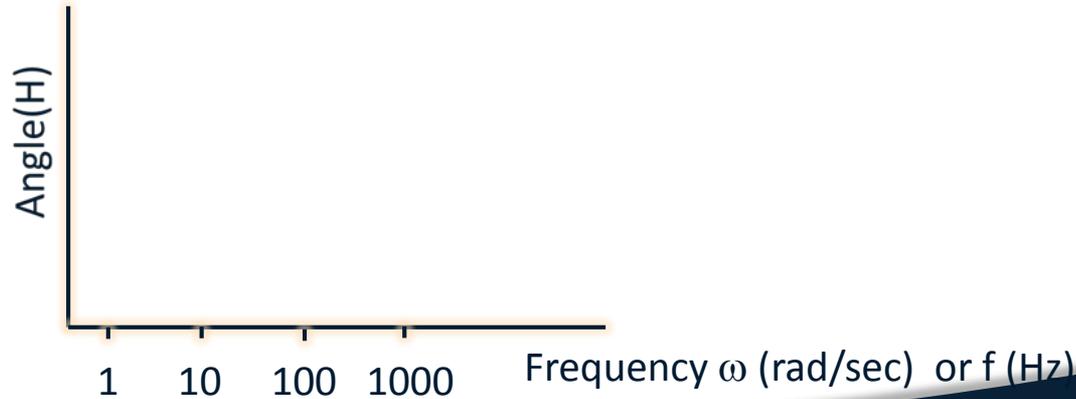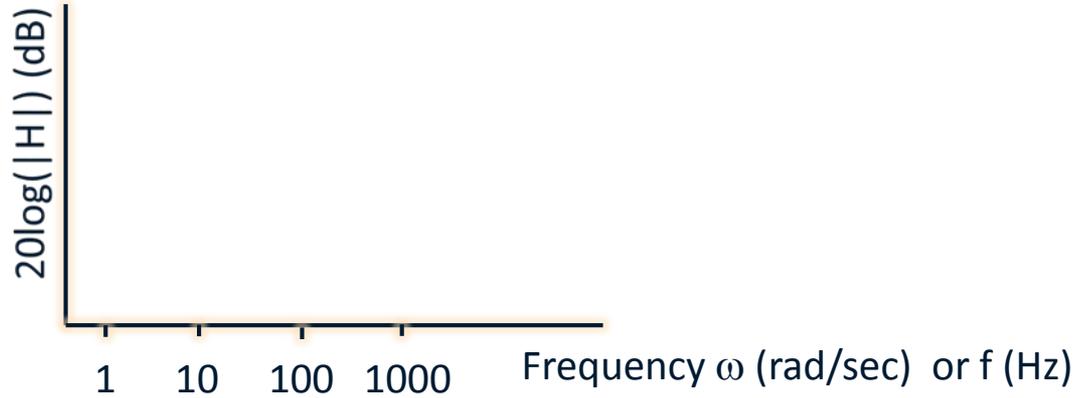

Linear Plot and Bode Plot

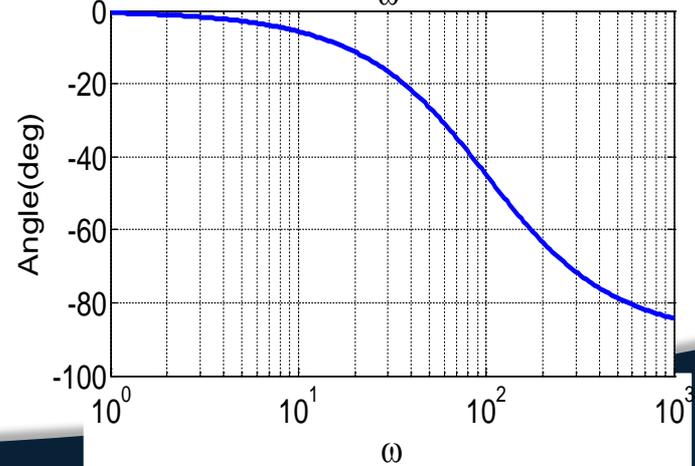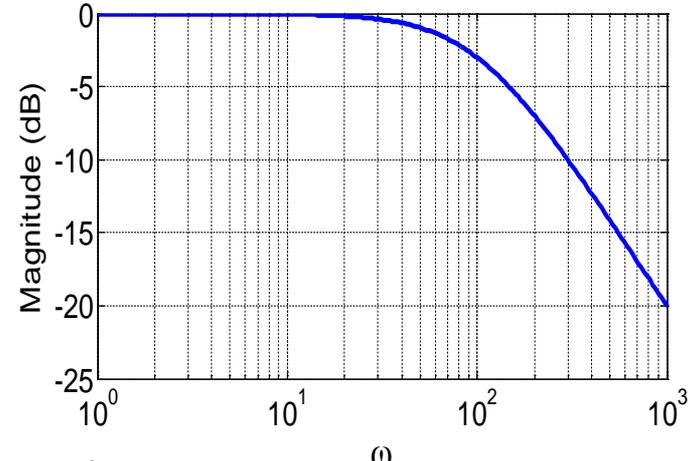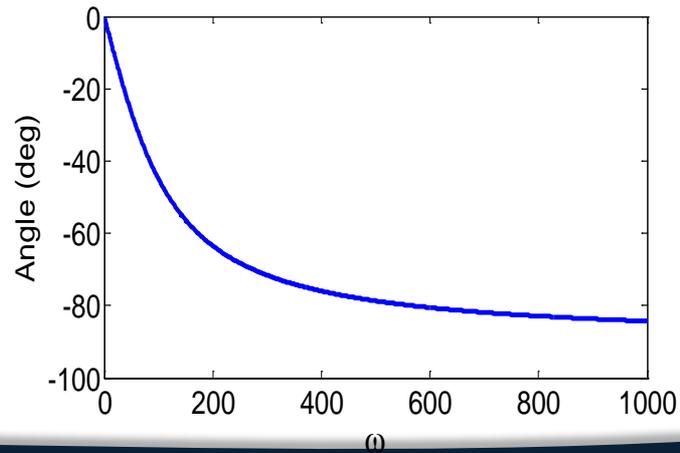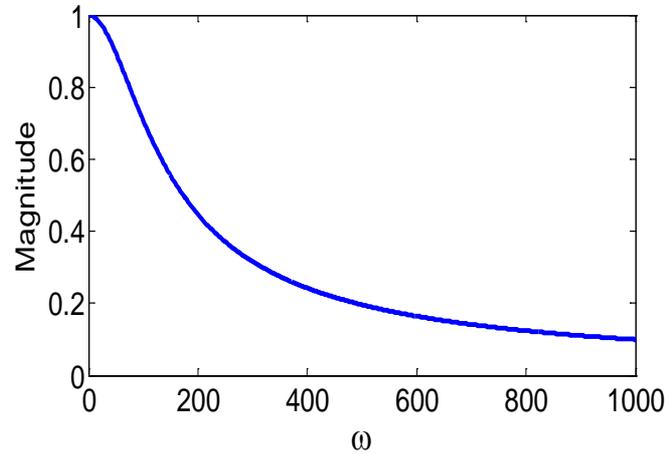

Bode Plot First-Order Characteristics


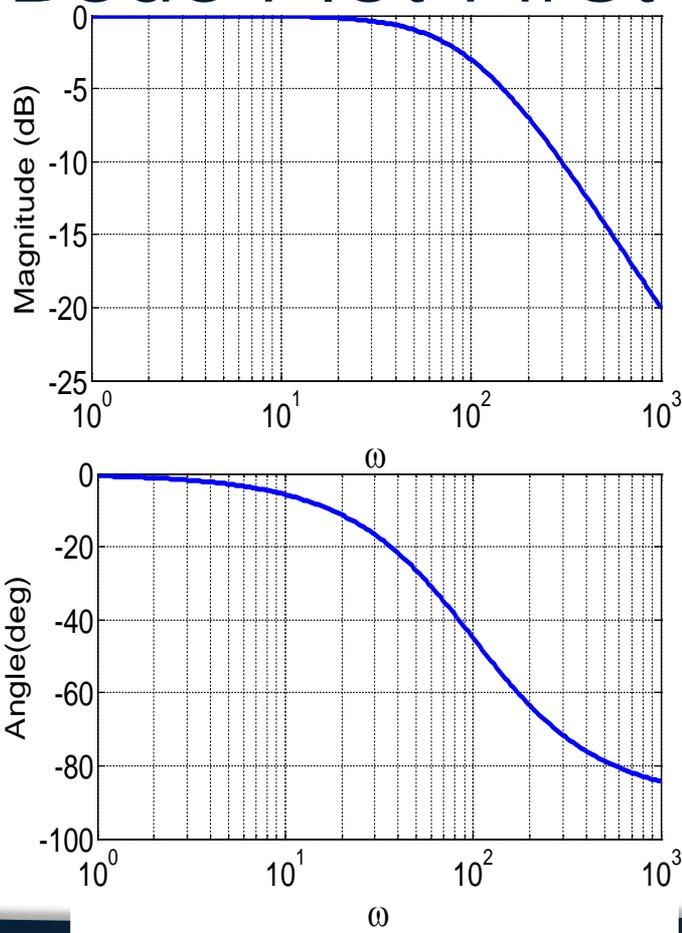


$$H(\omega) = \frac{1}{1 + j\omega RC}$$

$$|H(\omega)| = \frac{1}{\sqrt{1 + (\omega RC)^2}}$$


$$\angle H(\omega) = -a \tan(\omega RC)$$

Bode Plot of RLC Circuit, Overdamped

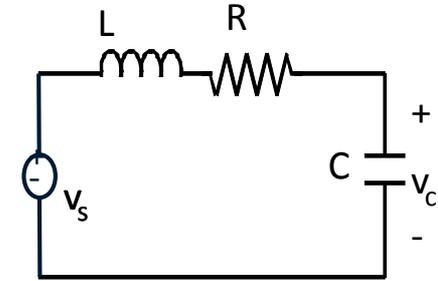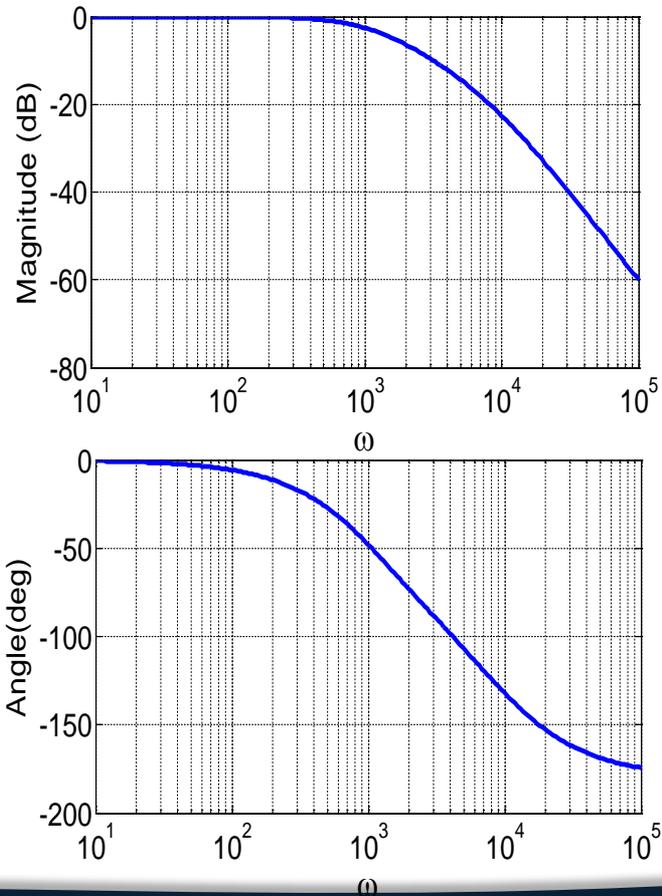

$$H(\omega) = \frac{1}{(1 - LC\omega^2) + RCj\omega}$$

Bode Plot of RLC Circuit, Underdamped

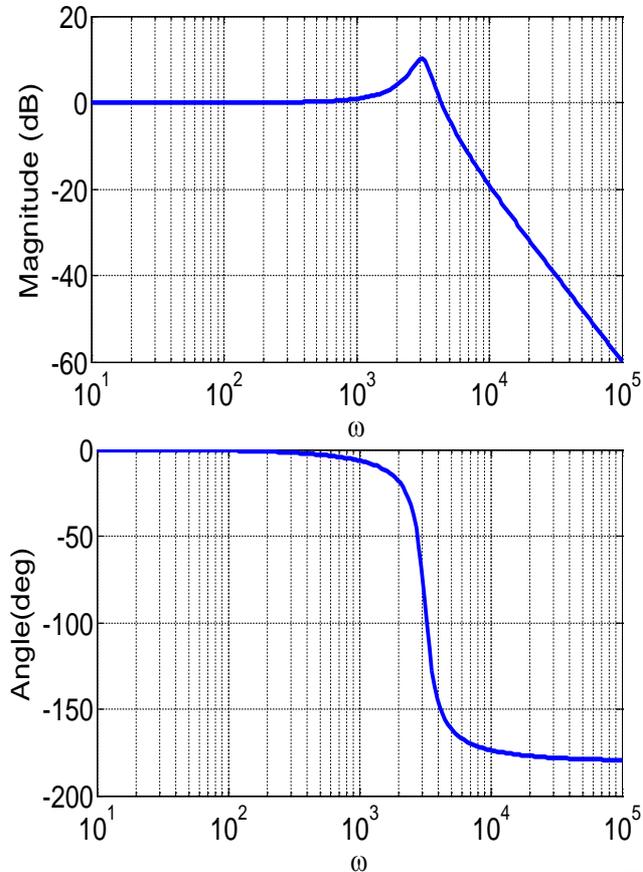

Summary

- ⦿ A **frequency response** is a plot of the transfer function versus frequency
- ⦿ The frequency response can be used to determine the steady-state sinusoidal response of a circuit at different frequencies