



**Dr. Bonnie H. Ferri**  
Professor and Associate Chair  
School of Electrical and  
Computer Engineering

# Introduction to Electronics

*An introduction to linear electric components and a study of circuits containing such devices.*

**TECH**



**Dr. Bonnie H. Ferri**  
Professor and Associate Chair  
School of Electrical and  
Computer Engineering

# Basic Op Amp Amplifier Configurations

*Introduce Inverting and Non-Inverting Amplifiers, Difference and Summing Amplifiers*

**TECH**


# Previous Lessons

- Op Amp Ideal Behavior and Buffer Circuits

# Lesson Objectives

- ⦿ Introduce
  - Inverting and Non-Inverting Configurations
  - Difference and Summing Configurations
- ⦿ Introduce the Gain of a circuit


# Non-Inverting Amplifiers

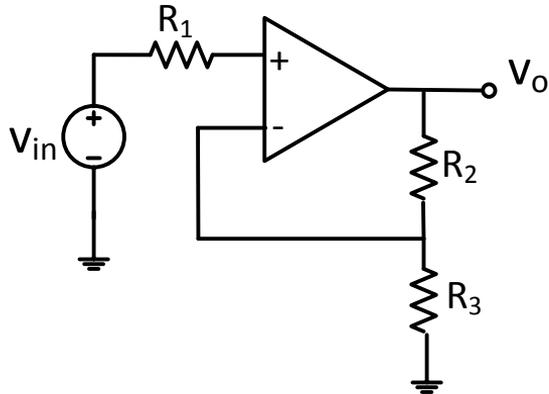

$$V_o = \frac{R_2 + R_3}{R_3} V_{in}$$

$$V_o = G V_{in} \quad \text{Gain: } G = \frac{R_2 + R_3}{R_3}$$


# Non-Inverting Amplifier Example

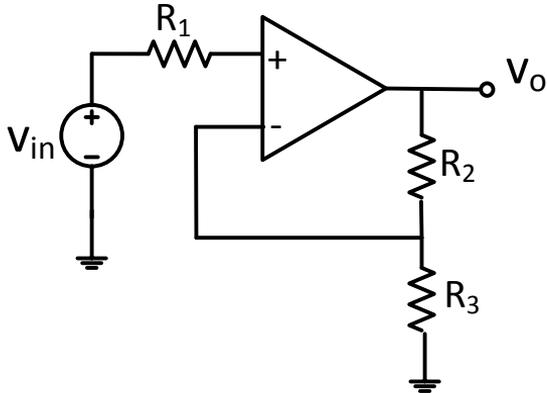

If  $R_2 = R_3 = 200\Omega$ ,

- Since,  $G > 1$ , the input is amplified
- If  $G < 1$ , the input is attenuated


# Inverting Amplifier

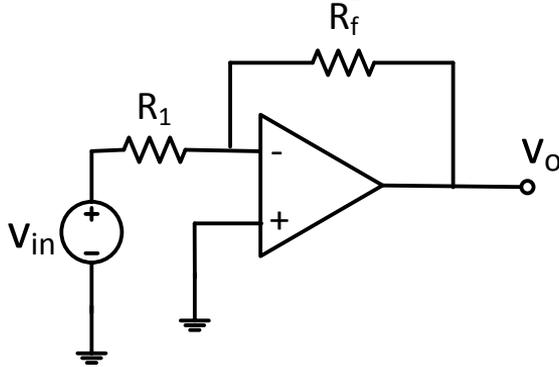

$$V_o = -\frac{R_f}{R_1} V_{in}$$

$$V_o = G V_{in}$$


# Inverting Amplifier Example

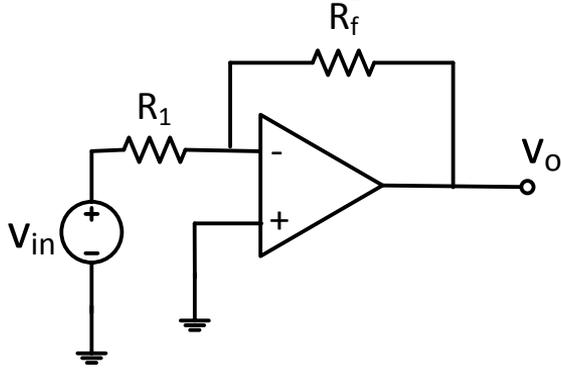

$$R_1 = 1000\Omega, R_f = 2000\Omega$$


- If  $G > 1$ , the input is amplified
- If  $G < 1$ , the input is attenuated

# Difference Circuit

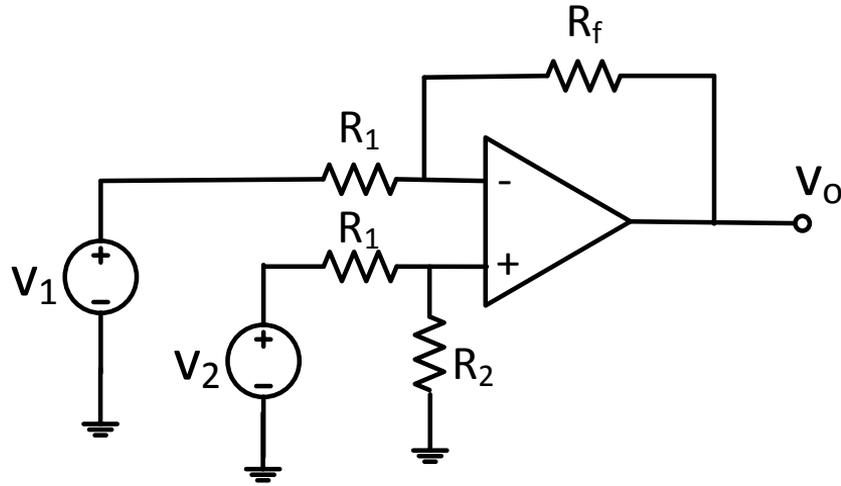


$$V_o = \frac{R_f}{R_1} (V_2 - V_1)$$

# Difference Circuit

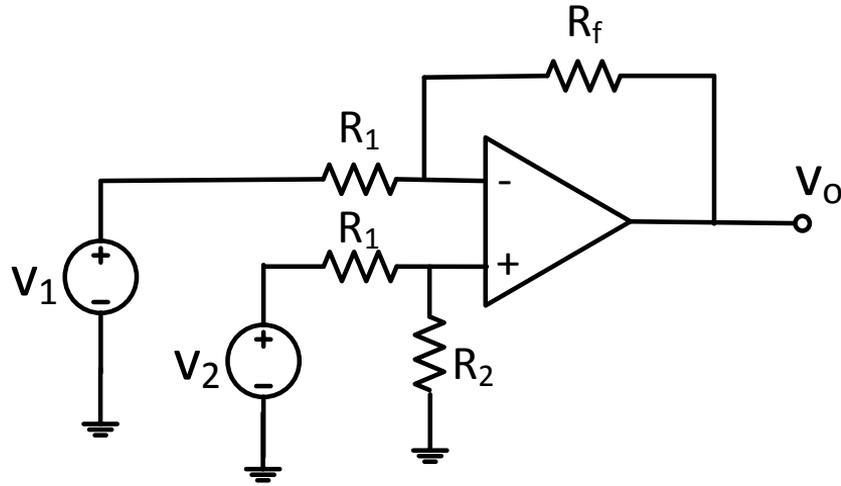

$$V_o = \frac{R_f}{R_1} (V_2 - V_1)$$

# Summing Amplifier

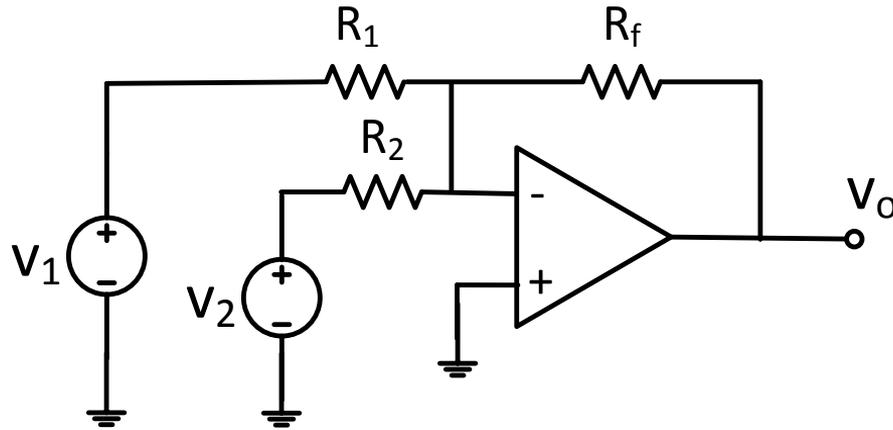

$$V_o = G_1 V_1 + G_2 V_2$$

$$G_1 = -\frac{R_f}{R_1} \quad G_2 = -\frac{R_f}{R_2}$$

# Summary

- Gain:  $V_o = GV_{in}$
- Amplifier Circuit Configurations
  - Non-Inverting Amplifier
  - Inverting Amplifier
  - Difference Amplifier
  - Summing Amplifier

# Next Lesson

- Differentiators and Integrators