



**Dr. Bonnie H. Ferri**  
Professor and Associate Chair  
School of Electrical and  
Computer Engineering

# Introduction to Electronics

*An introduction to linear electric components and a study of circuits containing such devices.*

**TECH**



**Dr. Bonnie H. Ferri**  
Professor and Associate Chair  
School of Electrical and  
Computer Engineering

# Differentiators and Integrators

*Introduce Integrating and Differentiating Op Amp Circuits*

**TECH**


# Previous Lesson

- Basic Op Amp Amplifier Configurations

# Lesson Objectives

- Introduce Differentiators and Integrators
- Demonstrate the performance of both circuits on an oscilloscope


# Differentiator Circuit

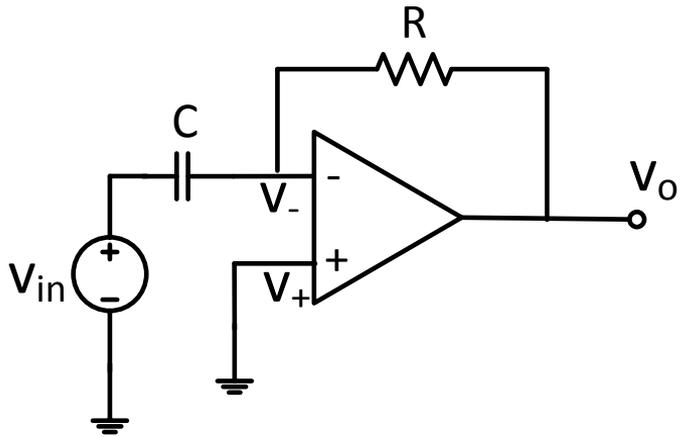

$$i = C \frac{dV_c}{dt} V_c$$

$$V_o = -RC \frac{dV_{in}}{dt}$$

# Differentiator Circuit


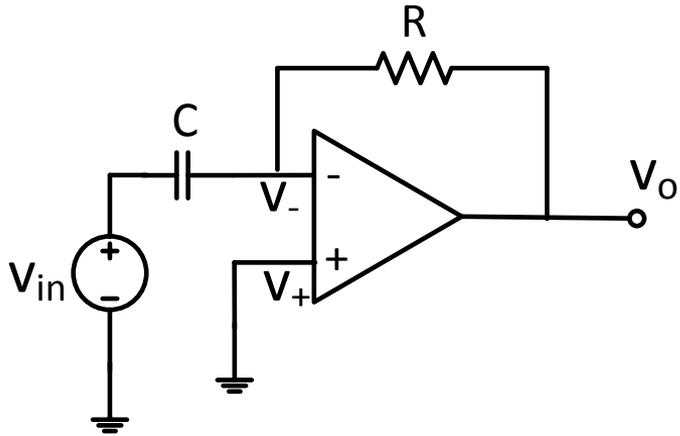


Derivation:


1. KVL:  $V_{in} = V_c + Ri + V_o$
2.  $V_{in} = V_c$
3.  $V_o = -Ri = -RC(dV_{in} / dt)$

$$V_o = -RC \frac{dV_{in}}{dt}$$

# Differentiator Example

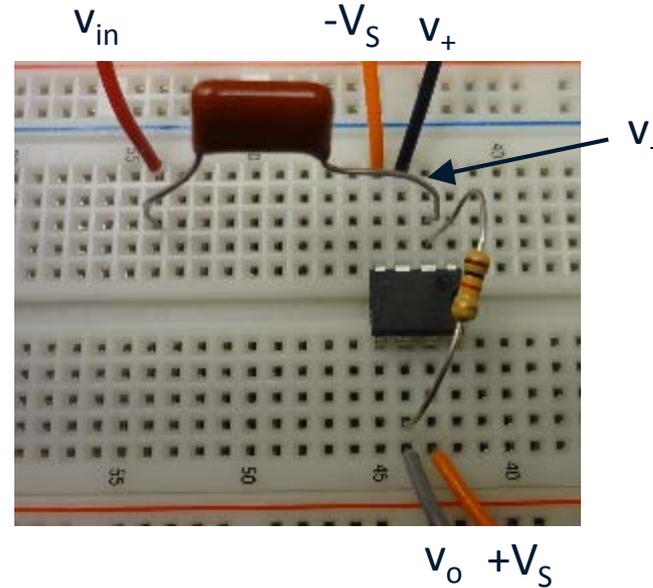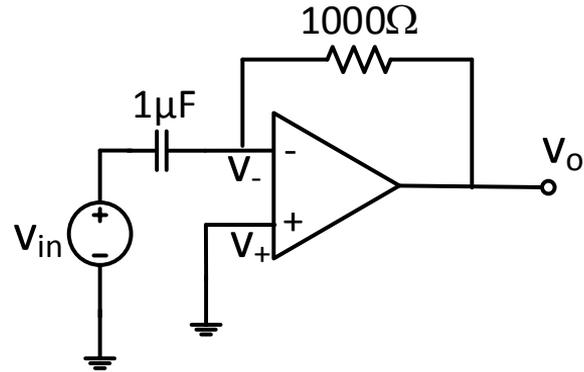


# Results

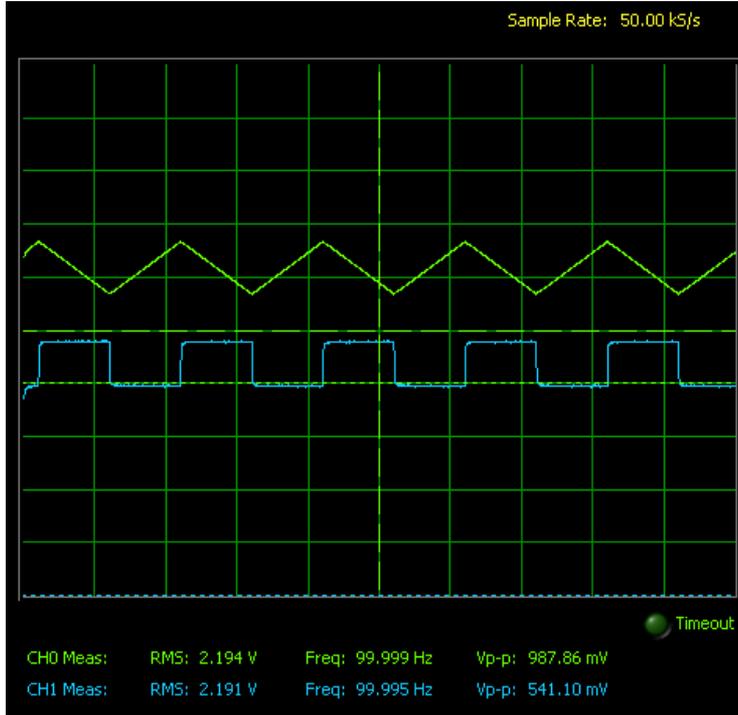

$$V_o = -RC \frac{dV_{in}}{dt}$$

# Integrator Circuit

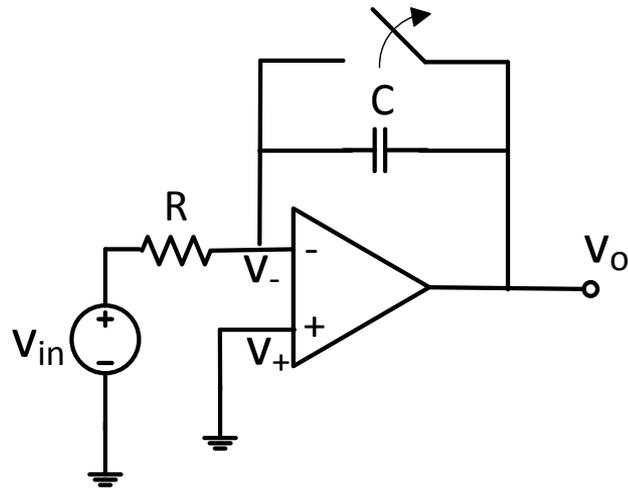


$$V_o = -\frac{1}{RC} \int_0^t V_{in} dt$$

$$i = C \frac{dV_c}{dt}$$

$$V_c = \frac{1}{C} \int_0^t i dt$$

# Integrator Circuit

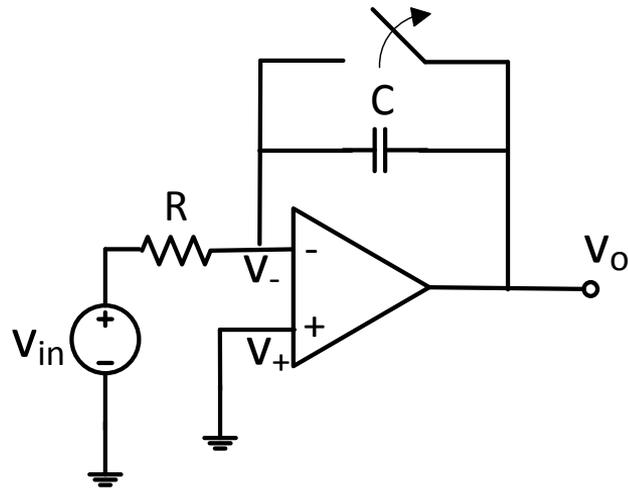

$$V_o = -\frac{1}{RC} \int_0^t V_{in} dt$$

$$i = C \frac{dV_c}{dt} \quad V_c = \frac{1}{C} \int_0^t i dt$$

Derivation:

For  $t < 0$ :  $V_{in} = iR$  and  $V_o = 0$



For  $t > 0$ :  $V_{in} = iR$        $i = V_{in}/R$

$V_{in} = iR + V_c + V_o$


$V_o = -V_c = -1/C \int_0^t V_{in}/R dt$



# Integrator Example

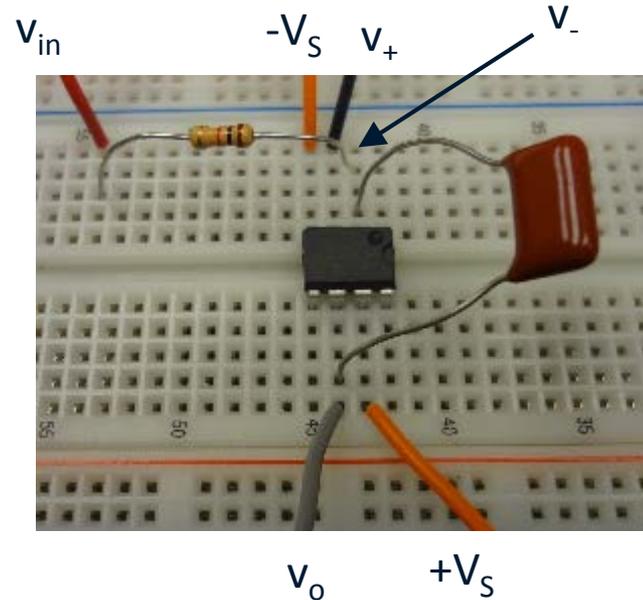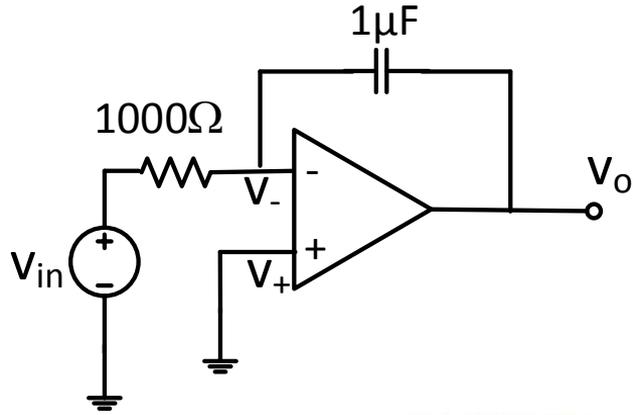

# Results

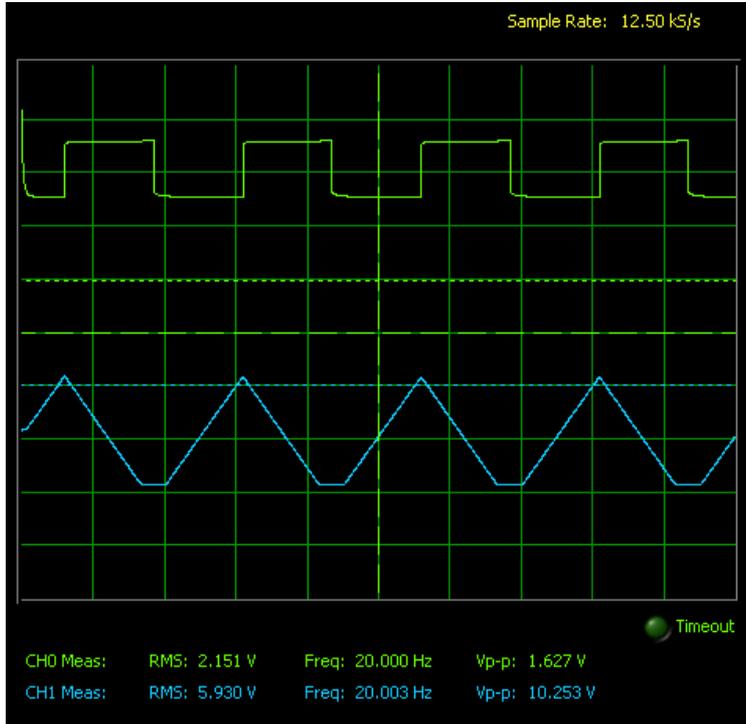

$$V_o = \frac{-1}{RC} \int_0^t V_{in} dt$$

# Summary

- ⦿ Differentiator and Integrator Op Amp circuits examined

# Next Lesson

- Active Filters