



**Dr. Bonnie H. Ferri**  
Professor and Associate Chair  
School of Electrical and  
Computer Engineering

# Introduction to Electronics

*An introduction to linear electric components and a study of circuits containing such devices.*

**TECH**



**Dr. Bonnie H. Ferri**  
Professor and Associate Chair  
School of Electrical and  
Computer Engineering

# Diode Behavior and Models

*Introduce ideal and non-ideal diode I-V curves*

**TECH**


# Previous Lesson

- ⦿ The physics of PN junctions


# Lesson Objectives

- ⦿ Analyze diode behavior
- ⦿ Introduce diode applications
- ⦿ Describe different operating regions
- ⦿ Introduce simple diode models that approximate the actual device

# Background

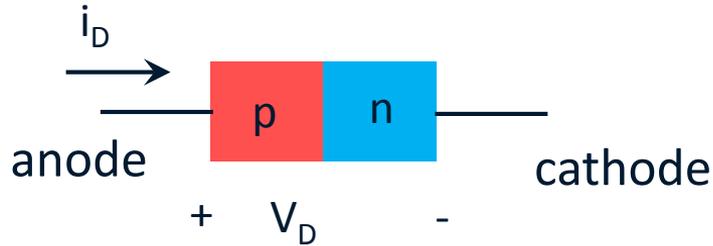




## Circuit Symbol:

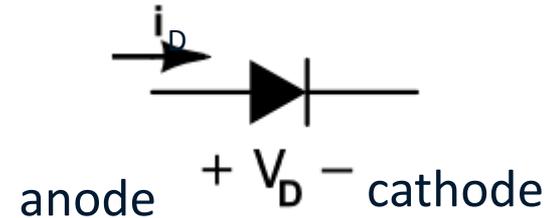


## Uses:

- **Block current flow** in a specific direction
- **Rectifier** (AC to DC conversion)
- **Voltage regulator** and **limiter** (protection)
- **Light Emitting Diodes** (LEDs)
- **AM Detectors**
- **Electronic tuners**
- **Photodiodes**


# I-V Characteristics

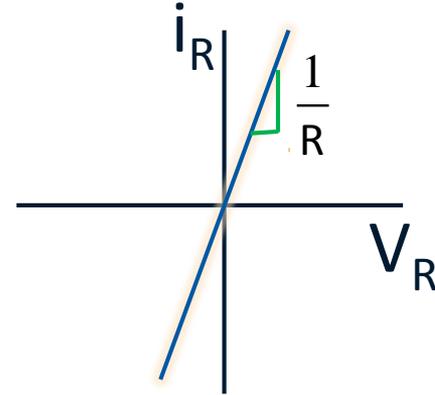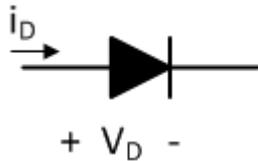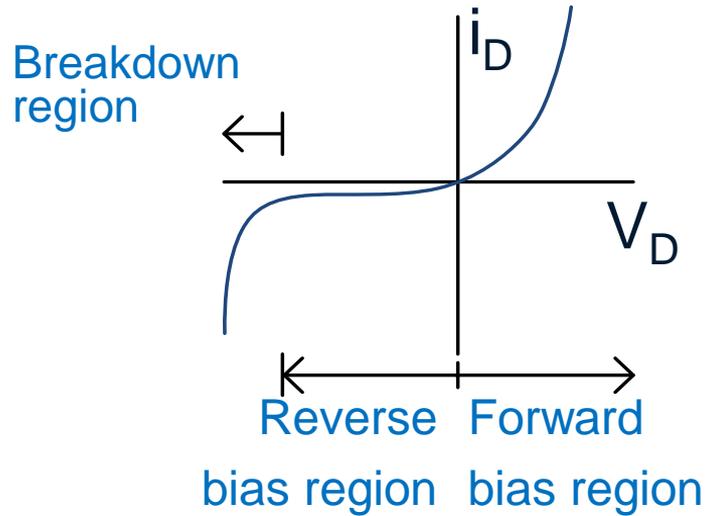


# Simple Diode Models

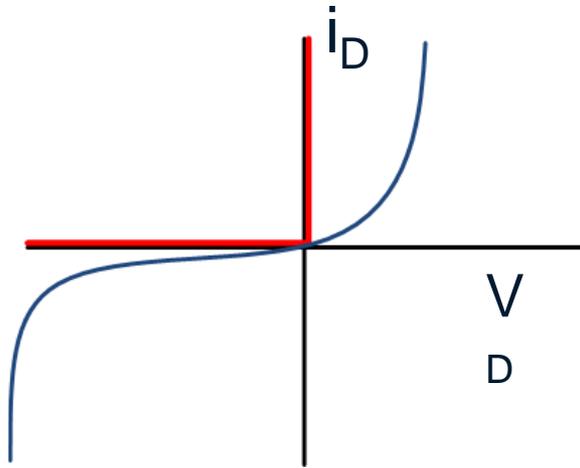

**Ideal Diode Model**


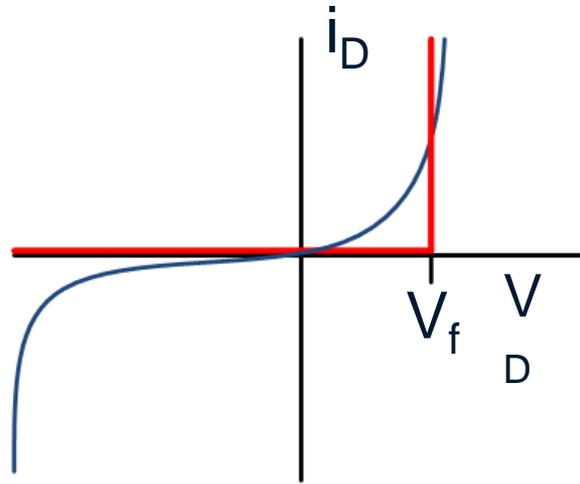


**Ideal Diode + Voltage Source Model**

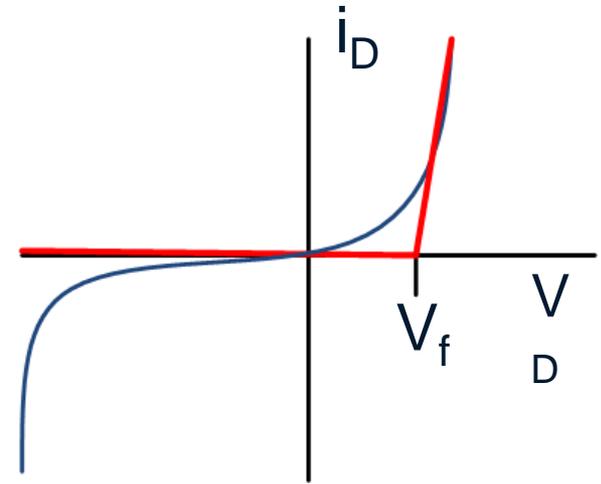

**Ideal Diode + Voltage Source + Resistor Model**

# Ideal Diode

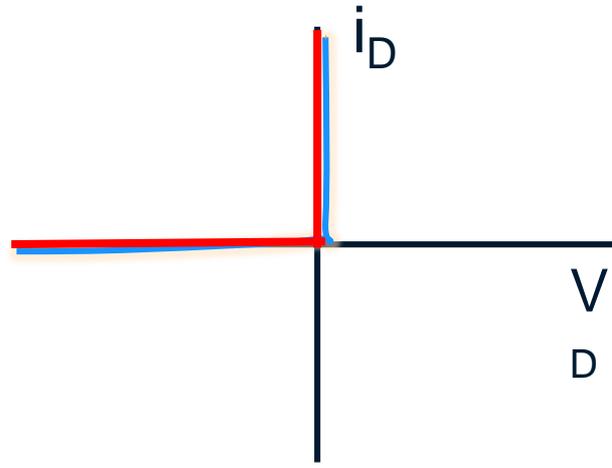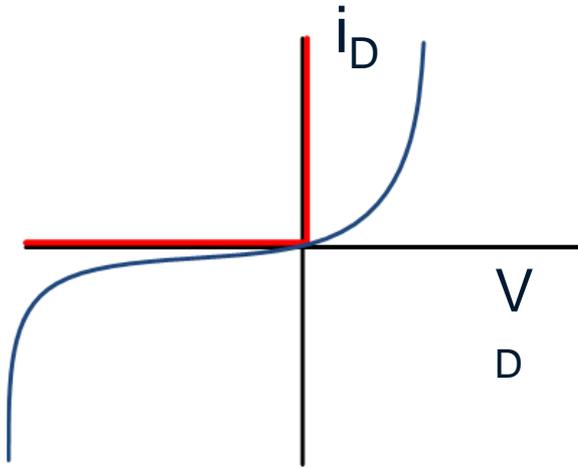

# Summary

- Diodes have three operating regions
  - Forward bias,  $i_D > 0$
  - Reverse bias,  $V_D < 0$
  - Breakdown
- Ideal diodes only allow current to flow in one direction
- Three models: ideal, ideal + voltage source, ideal + voltage source + resistor

# Next Lesson

- Ideal diode behavior