



Dr. Bonnie H. Ferri
Professor and Associate Chair
School of Electrical and
Computer Engineering

Introduction to Electronics

An introduction to linear electric components and a study of circuits containing such devices.

TECH



Dr. Bonnie H. Ferri
Professor and Associate Chair
School of Electrical and
Computer Engineering

Assumed States Method

Introduce ideal diode circuits with multiple diodes

TECH

Previous Lesson

- Circuit Analysis with a single ideal diode



Lesson Objective

- Describe the procedure for handling multiple diodes in a single circuit

Assumed States Procedure

- 1) Identify all possible diode state combinations
 - 1 diode \Rightarrow 2 states
 - 2 diodes \Rightarrow 4 states
 - 3 diodes $\Rightarrow 2^3 = 8$ states
- 2) Analyze each state by replacing the diodes with the corresponding open or short.
- 3) Determine which state is consistent:
 - ON: $i_D > 0$
 - OFF: $V_D < 0$

Example

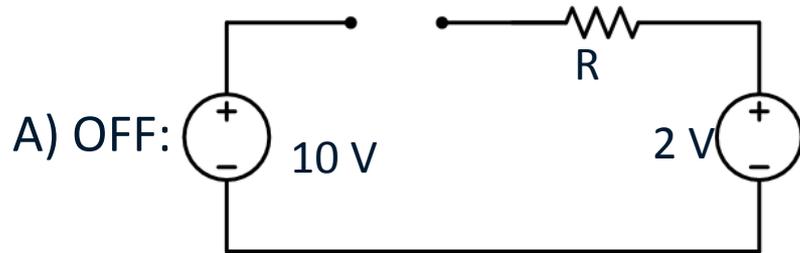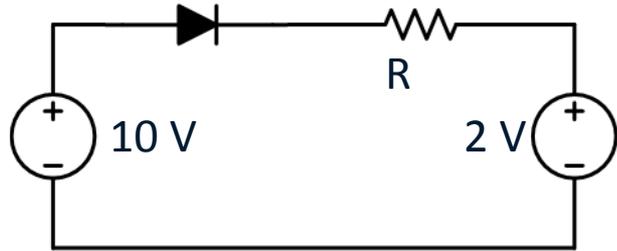

States	D1	Consistent?
A	OFF	
B	ON	


$$-10 + V_D + 2 = 0, V_D > 0$$

(not consistent)

$$-10 + i_D 1k + 2 = 0, i_D = 0.008A > 0$$


(consistent)

Two Diode Example

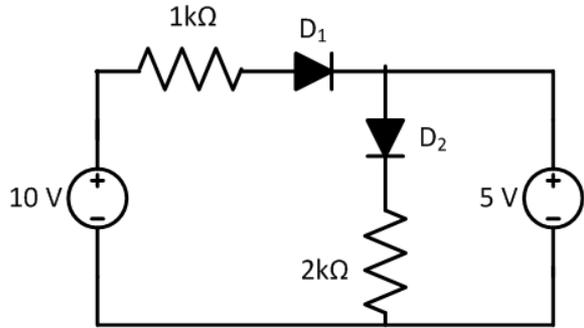


Find V_1

States	D1	D2	Consistent?
A	OFF	OFF	
B	OFF	ON	
C	ON	OFF	
D	ON	ON	

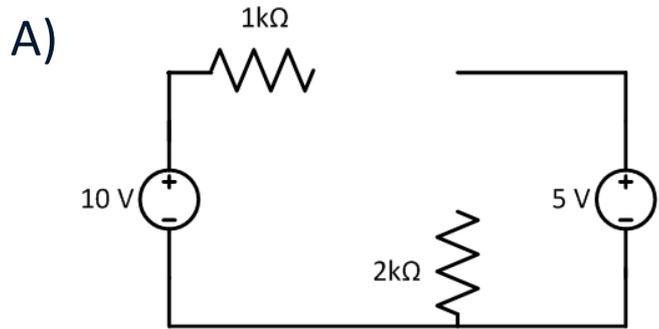

KVL: $-5 + V_{D2} = 0 \implies V_{D1} = 5 > 0$
(Not consistent)



Example continued

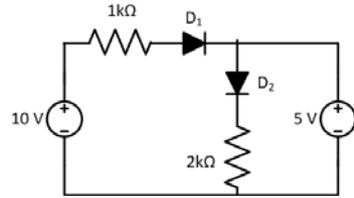


KVL: $-10 + V_{D1} + 5 = 0$, $V_{D1} = 5V > 0$
(Not consistent)

$V_{D2} = 5V > 0$
(Not consistent)

States	D1	D2	Consistent?
A	OFF	OFF	No
B	OFF	ON	
C	ON	OFF	
D	ON	ON	

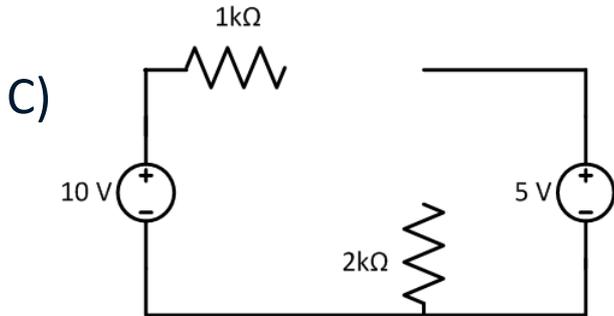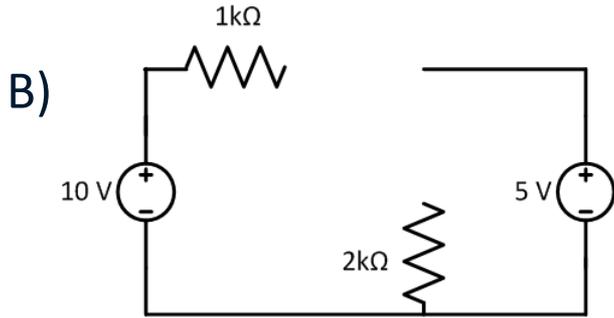

Example continued

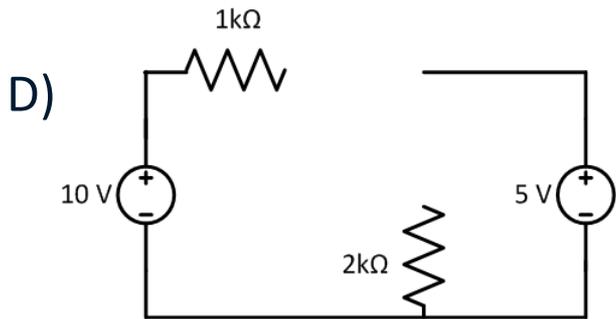


$$\text{KVL: } -10 + 1000i_{D1} + 5 = 0$$

$$i_{D1} = 0.005\text{A} > 0$$

$$i_{D2} = 5/2000 > 0$$

(Consistent)

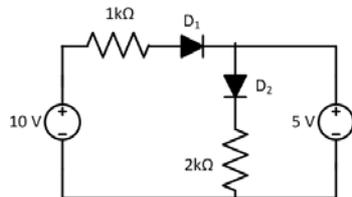

Operating state:

D_1 and D_2 are ON

$$V_1 = 1000(0.005) = 5\text{V}$$

States	D1	D2	Consistent?
A	OFF	OFF	No
B	OFF	ON	No
C	ON	OFF	No
D	ON	ON	

Summary

- ⦿ Diodes act as a short or an open, depending on the bias
- ⦿ When solving a circuit, assume each possible state, and check to see if the behavior is consistent with that state

Next Lesson

- Ideal Diode with a Voltage Source