

Introduction to Electronics



Dr. Bonnie H. Ferri
Professor and Associate Chair
School of Electrical and
Computer Engineering

An introduction to electronic components and a study of circuits containing such devices.

TECH

CMOS Logic Gates



Dr. Bonnie H. Ferri
Professor and Associate Chair
School of Electrical and
Computer Engineering

Introduction to logic gates made from CMOS transistors

TECH




Previous Lesson

- MOSFET Switches

Lesson Objectives

- Introduce logic gates and their transistor circuits
 - NOT, NAND, NOR, AND, OR

CMOS NOT Gate (Inverter Circuit)



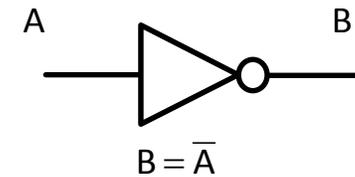
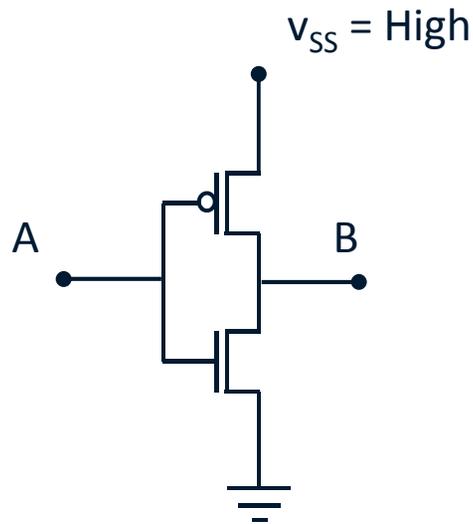
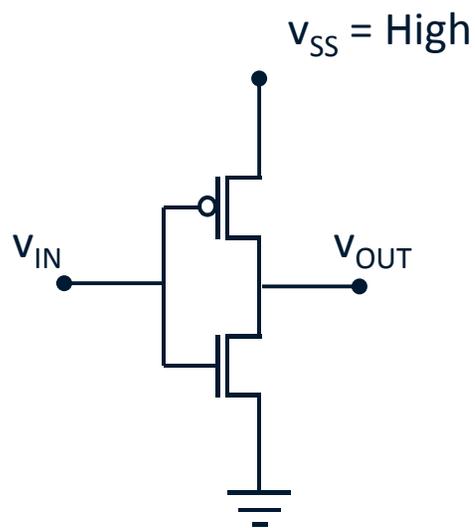


Truth Table

V_{IN}	V_{OUT}
High	Low
Low	High


A	B
0	1
1	0

Logic Gates

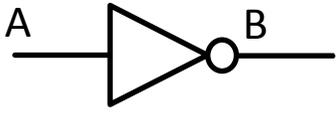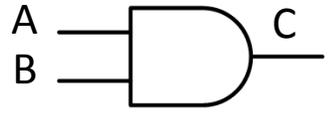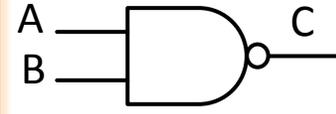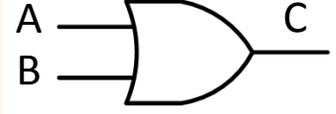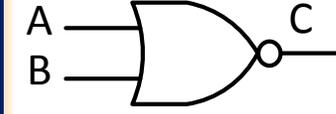NOT		AND		NAND		OR		NOR	
A	B	A B	C	A B	C	A B	C	A B	C
0	1	00	0	00	1	00	0	00	1
1	0	01	0	01	1	01	1	01	0
		10	0	10	1	10	1	10	0
		11	1	11	0	11	1	11	0
 <p>$B = \bar{A}$</p>		 <p>$C = A \bullet B$</p>		 <p>$C = \overline{A \bullet B}$</p>		 <p>$C = A + B$</p>		 <p>$C = \overline{A + B}$</p>	


PMOS Switch Behavior

NMOS

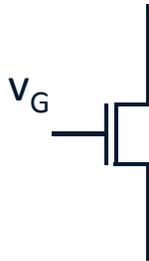

V_G	Switch
High	ON
Low	OFF

PMOS



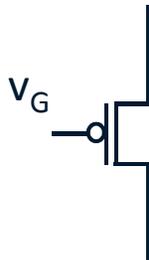


V_G	Switch
High	OFF
Low	ON

NAND Gate

NAND




A	B	C
0	0	1
0	1	1
1	0	1
1	1	0

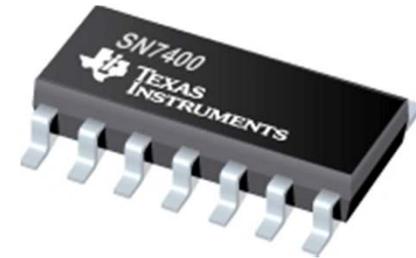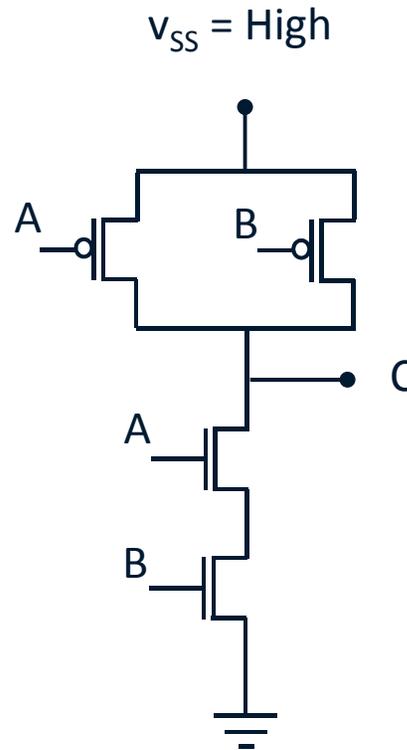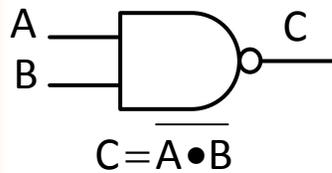

NOR Gate

NOR

A	B	C
0	0	1
0	1	0
1	0	0
1	1	0

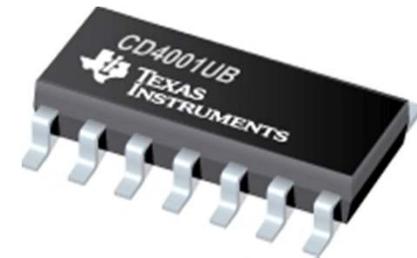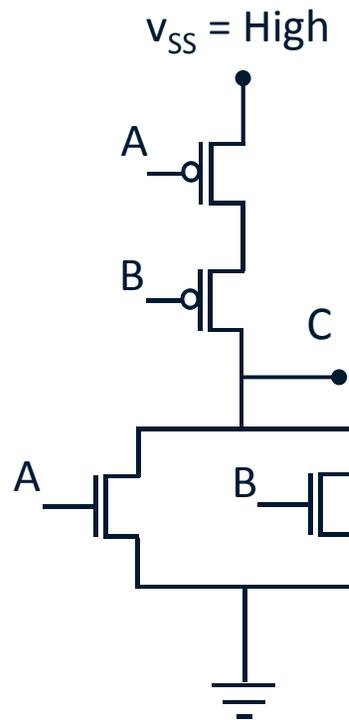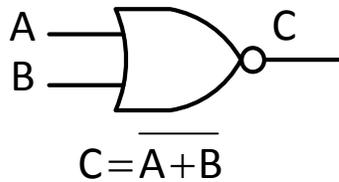

Summary

- ⦿ Logic gate circuits are made from CMOS n-type and p-type transistors

Next Lesson